

A Fully Compositional Theory of Digital Circuits

George Kaye


University of Birmingham

21 June 2024

Applied Category Theory 2024 (ACT 2024)


What are we going to be talking about?

Digital circuits!

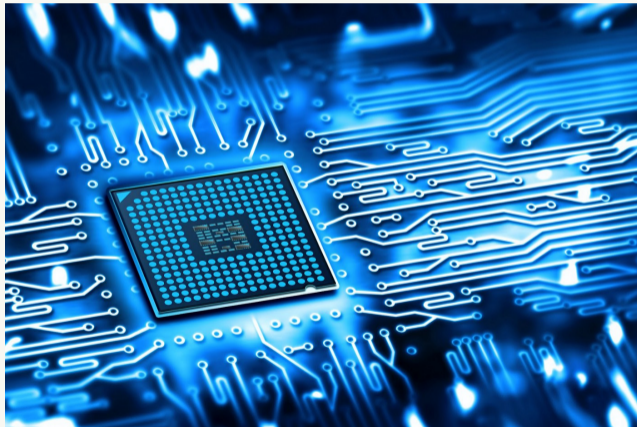


What are we going to be talking about?

Digital circuits!

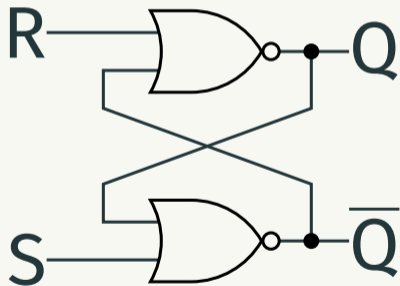

What are we going to be talking about?

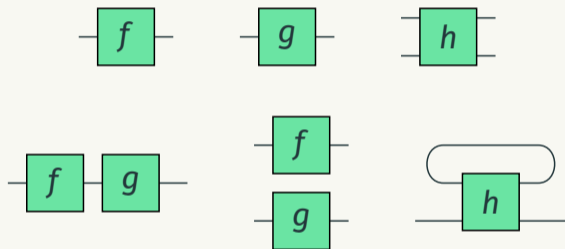We want a **compositional** theory of digital circuits.



Using **string diagrams** removes
much of the bureaucracy

(also they look pretty)

How did we get here?



2003



Yves Lafont

'Towards an algebraic theory of Boolean circuits'

2016



Dan Ghica, Achim Jung, Aliaume Lopez

'Diagrammatic semantics for digital circuits'

2019

The story so far




'Do you know category theory'
'Do you want to do circuits stuff'



'No'
'Okay'

David Sprunger

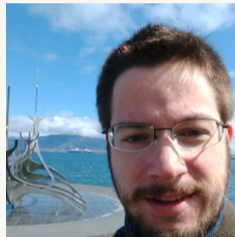

'I will help too'

Hold on a second...




Hold on a second...




Syntax

Combinational circuit components


gates

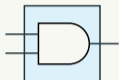

AND gate

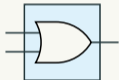

OR gate

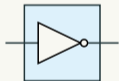

NOT gate

(co)monoid structure



introduce



fork



join



eliminate


categorical structure



identity





symmetry

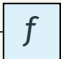Light circuits  only contain gates and structure.


(actually, we do it more generally than this, but let's keep it simple)

Sequential circuit components


Values

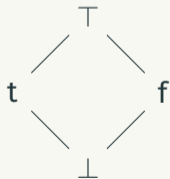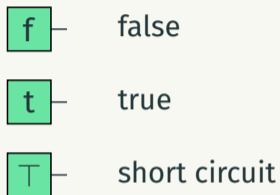

Delay

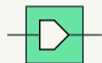


Feedback

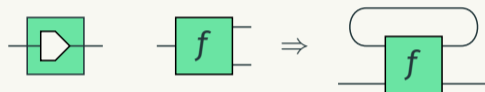

Dark circuits may contain
delay or feedback.

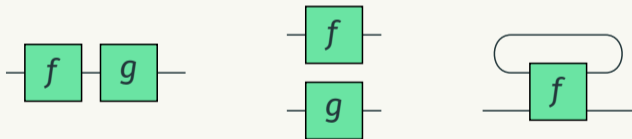
Circuits are morphisms in a **freely generated symmetric traced monoidal category (STMC)**.



Why not use Frobenius structure?



We want copying...

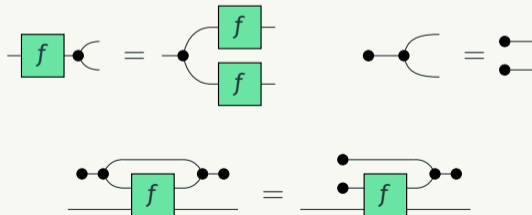

Where were we?



What is the meaning?

What are the **denotational semantics** of digital circuits?


Certain kinds of **stream functions**!

$$f(v_0 :: v_1 :: v_2 :: \dots) = w_0 :: w_1 :: w_2 :: \dots$$

Denotational equivalence

$$\llbracket \boxed{f} \rrbracket = \llbracket \boxed{g} \rrbracket \Rightarrow \boxed{f} \approx \boxed{g}$$

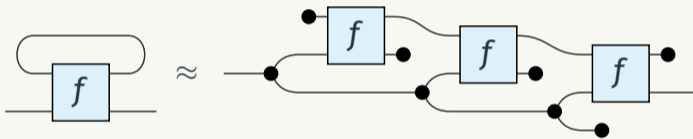We can also eliminate non-delay-guarded feedback



(Kleene fixpoint theorem)

Denotational equivalence obscures the **structure** of terms

We want to reason more **syntactically**

Operational semantics Algebraic semantics

a bit has changed

(pretty much) new


Suppose we have two circuits
with the same denotation

$$\llbracket \text{---} \boxed{f} \text{---} \rrbracket = \llbracket \text{---} \boxed{g} \text{---} \rrbracket$$

What does this tell us about the
structure of these circuits?




We want to find a set of
reductions for digital circuits

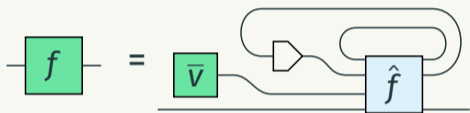We want to reduce circuits to their outputs
syntactically in a **step-by-step** manner



by moving boxes and wires around

Going global

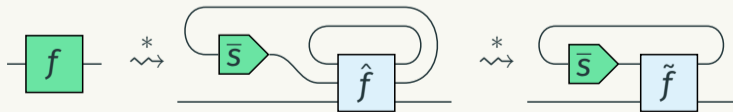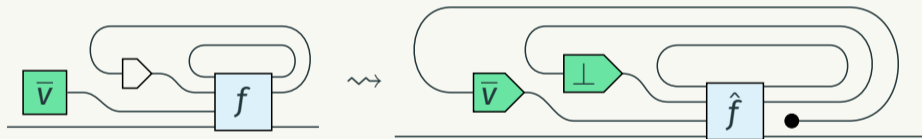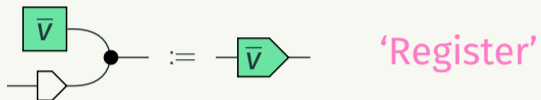


What is the goal

We want to compute the **outputs** of circuits given some **inputs**



How does a circuit **process** a value?


Reducing values

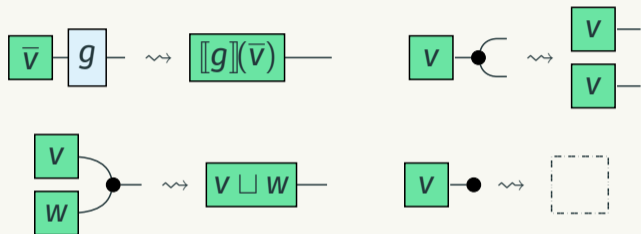


Lemma

For every f there exists \bar{w} s.t. $\bar{v} \text{---} f \text{---} \overset{*}{\rightsquigarrow} \bar{w} \text{---} .$

What about **delays**?

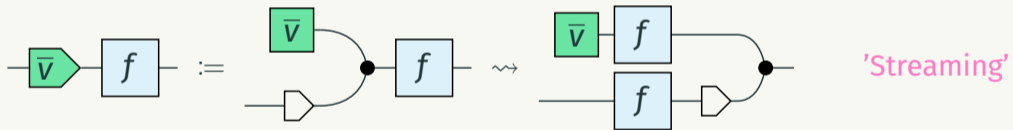

Catching the jet stream

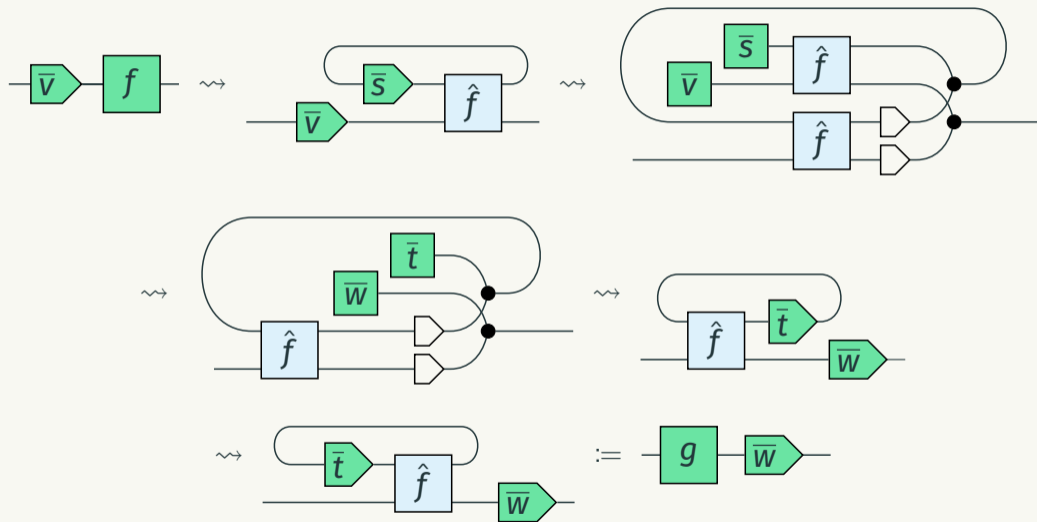

When are two circuits **observationally equivalent**?

Circuits have **finitely many states**...



Maximum number of states: $|\mathbf{V}|$ number of delays

Observe this




Two circuits are **observationally equivalent** if the reduction procedure creates the same outputs for all inputs of length $|\mathbf{V}|^{\text{max number of delays}} + 1$.

$$\boxed{f} \approx \boxed{g} \Leftrightarrow \boxed{f} \sim \boxed{g}$$

Denotational semantics \cong Operational semantics

This operational semantics is a bit **different** to some others...

(cf. signal flow graphs)


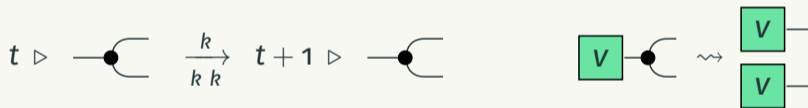


We want to **transform** the circuit


This is a **superexponential** upper bound for testing circuit equivalence

Can we do better?

First things first...


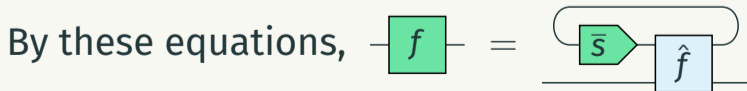
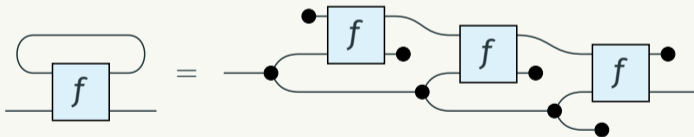


Say we have a procedure $\|_-\|$ for establishing a **canonical circuit** for a function $f: \mathbf{V}^m \rightarrow \mathbf{V}^n$


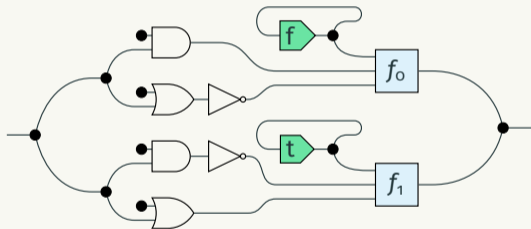


A circuit is **normalised** if it is in the image of $\|_-\|$

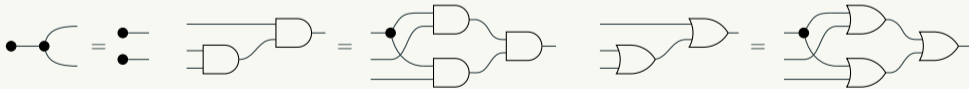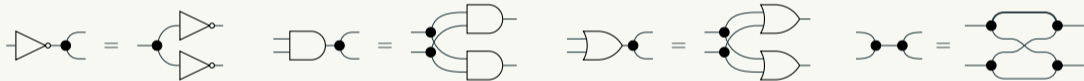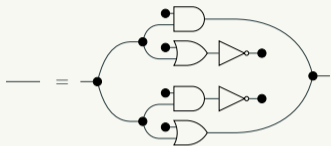

It's completely normal

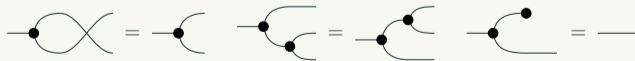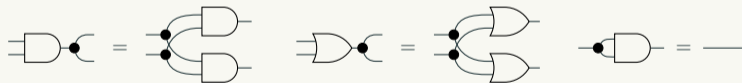

It's completely normal



Changing the states




How to translate between  and  ?

First **encode** one set of states into the other




(and for any future states)



Changing the states

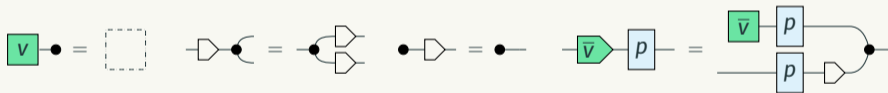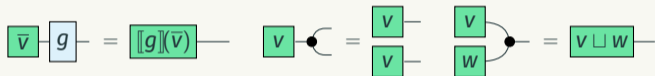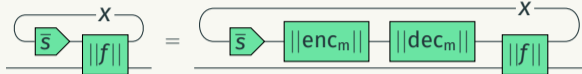

With these equations we can derive

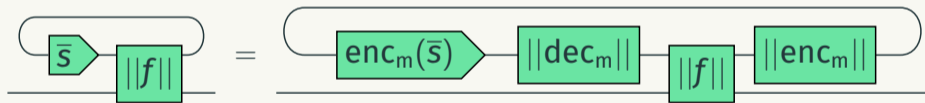


Is this enough?

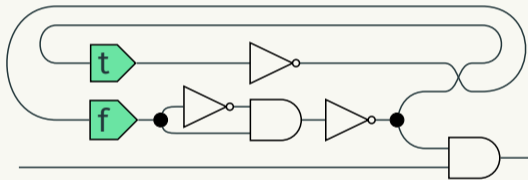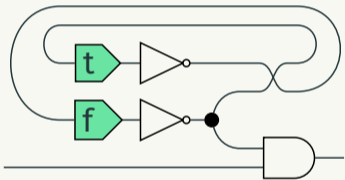

The cores may **not** have the same semantics!

Think about what matters

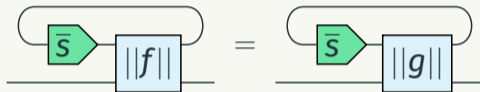

where f and g 'agree on the states that matter'

$$\boxed{f} \approx \boxed{g} \Leftrightarrow \boxed{f} = \boxed{g}$$

Denotational semantics \cong Algebraic semantics

Three different semantics for sequential digital circuits

